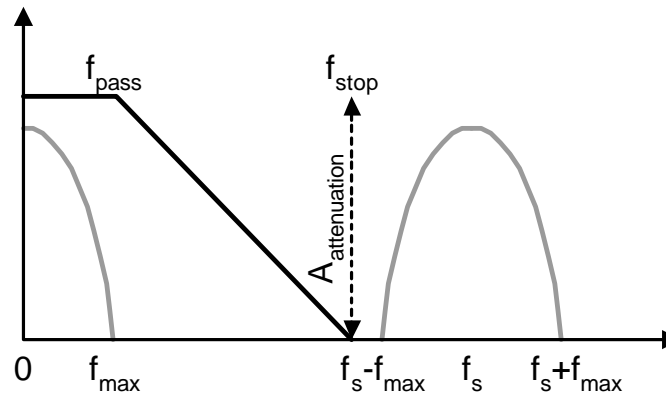

Discrete-Time Filter (Switched-Capacitor Filter)

Discrete-Time Filters

- Anti-Aliasing Filter & Smoothing Filter



- FIR Filters

- Windowing (Kaiser), Optimization

- IIR Filters

- Frequency Transformation from C-T Filters

- Forward / Backward Euler Transformation

- Bilinear Transformation

- Lossless Discrete Integrator (LDI) Transformation

SC Circuit Motivation

- **Active RC Filter**


- RC Time-Constant Variation ~ 30%
- Capacitance Ratio Variation ~ 0.1%

- **Building Blocks Well Integrated**

- Operational Amplifier : Folded-Cascode Configuration
- Capacitor : Poly1-Poly2, Metal-Metal
- Switches : Transmission Gate
- Multi-Phase Non-Overlapping Clocks



Folded-Cascode Op Amp

 

- Single-Stage Op Amp

- Frequency Compensation
by Load Capacitance C_L

- DC voltage gain

$$A_V(0) = g_{m1} \cdot R_{out} \approx g_{m1} \cdot [g_m r_{ds}^2]$$

- Unity-Gain Frequency

$$\omega_{0dB} = g_{m1}/C_L$$

- Slew Rate

$$SR = I_0/C_L$$


- Fully Differential Version

SC Circuit Applications

- **Analog Discrete-Time Filters**
- **Analog Discrete-Time Signal Processing Circuits**
 - Voltage Amplifiers, VGA
 - Interpolators, Decimations
 - Modulators, Demodulators, Mixers
 - Oscillators, Waveform Generators,
- **Data Transceivers : Telecom IC, CODEC, Baseband Processors, ...**
- **Data Converters**
 - DAC : Charge-Redistribution, Cyclic (Algorithmic)
 - ADC : Successive Approximation, Cyclic (Algorithmic), Pipeline
 - Sigma-Delta Modulators
- **Other Areas**



Basic Idea of SC Circuits

 

- Charge Transfer ($V_1 \Rightarrow V_2$)

$$\Delta Q = Q_1 - Q_2 = C \cdot (V_1 - V_2)$$


- Average Current during T

$$I_{avg} \equiv \frac{\Delta Q}{T} = \frac{C \cdot (V_1 - V_2)}{T}$$

- Equivalent Resistance

$$R_{eq} \equiv \frac{V_1 - V_2}{I_{avg}} = \frac{C}{T} = \frac{1}{Cf_S}$$

RC vs SC Integrators

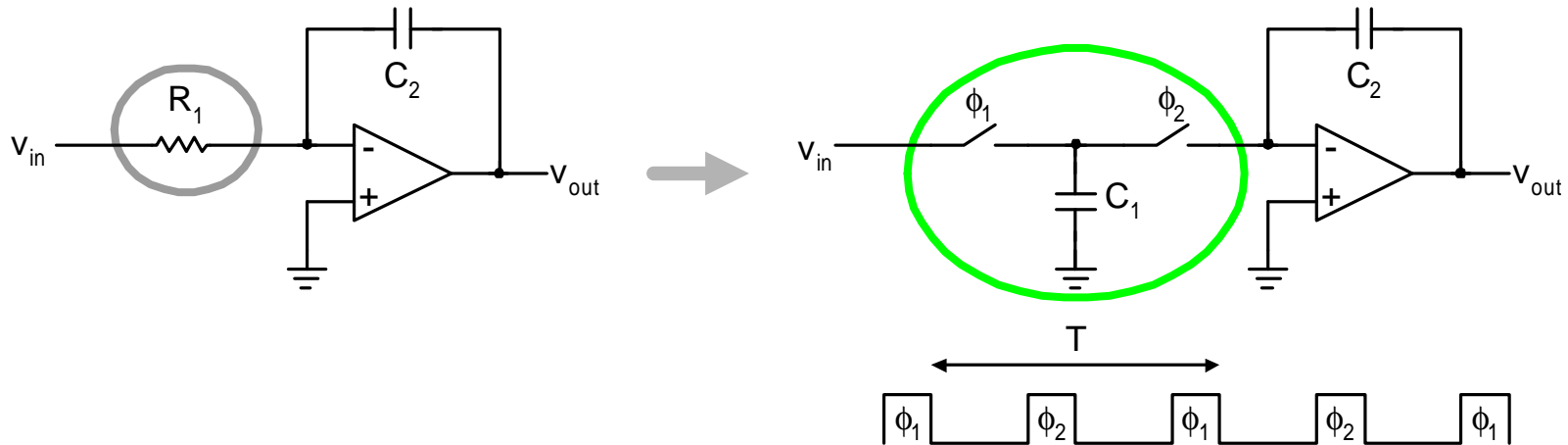


- **Passive Resistor → Switched-Capacitor Branch**

$$v_{\text{out}}(t) = -\frac{1}{R_1 C_2} \int_{-\infty}^t v_{\text{in}}(\tau) d\tau \Rightarrow H_a(s) \equiv \frac{V_{\text{out}}(s)}{V_{\text{in}}(s)} = -\frac{1}{R_1 C_2} \cdot \frac{1}{s}$$

- **Requirements**

$$C_1 = \frac{T}{R_1}$$


SC Integrator Operations

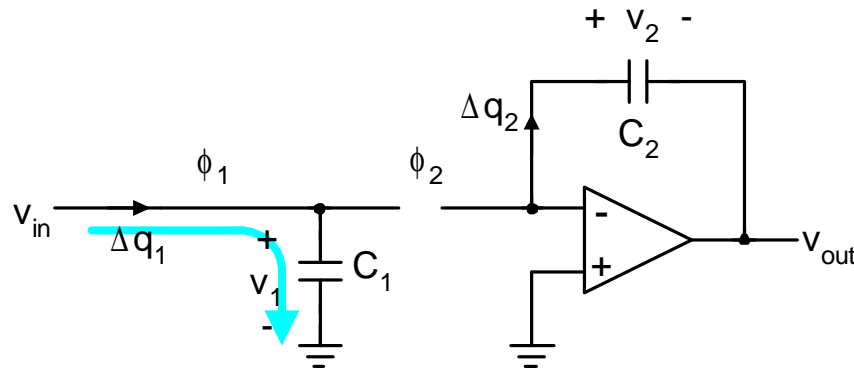

• $f_1 = 1$

$$q_1(n) = C_1 \cdot v_1(n) = C_1 \cdot v_{in}(n)$$
 
$$q_2(n) = C_2 \cdot v_2(n) = C_2 \cdot [0 - v_{out}(n)]$$



• $f_2 = 1$

$$q_1(n) = C_1 \cdot v_1(n) = C_1 \cdot 0$$

$$q_2(n) = C_2 \cdot v_2(n) = C_2 \cdot [0 - v_{out}(n)]$$


- at the integration time ($f_2 = 1$) \rightarrow n , ($f_1 = 1$) \rightarrow $n-1$, $Dq_1 = Dq_2$

$$\Delta q_1(n) = q_1(n) - q_1(n-1) = 0 - \{-C_1 \cdot v_{in}(n-1)\}$$

$$\Delta q_2(n) = q_2(n) - q_2(n-1) = C_2 \cdot [0 - v_{out}(n)] - C_2 \cdot [0 - v_{out}(n-1)]$$

$$\therefore C_2 \cdot [v_{out}(n) - v_{out}(n-1)] = -C_1 \cdot v_{in}(n-1)$$

Basic SC Integrator 1

 


$$\Delta q_1 = C_1 \cdot [0 - \{-v_{in}(n-1)\}]$$

$$\Delta q_2 = C_2 \cdot [v_2(n) - v_2(n-1)]$$


$$= -C_2 \cdot [v_{out}(n) - v_{out}(n-1)]$$

$$C_1 \cdot z^{-1} V_{in}(z) = -C_2 \cdot [1 - z^{-1}] \cdot V_{out}(z)$$
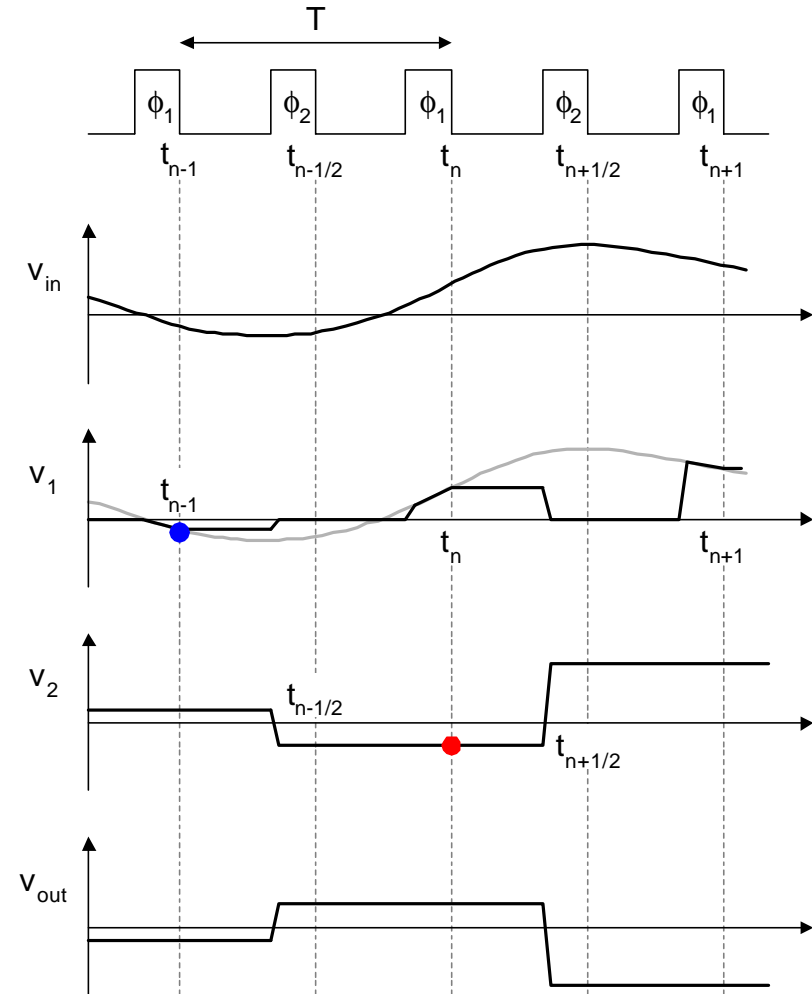
$$\therefore H(z) \equiv \frac{V_{out}(z)}{V_{in}(z)} = -\frac{C_1}{C_2} \cdot \frac{z^{-1}}{1 - z^{-1}}$$



Basic Integrator 2

 


$$\Delta q_1 = C_1 \cdot [v_{in}(n) - 0]$$

$$\Delta q_2 = C_2 \cdot [v_2(n) - v_2(n-1)]$$

$$= -C_2 \cdot [v_{out}(n) - v_{out}(n-1)]$$

$$C_1 \cdot V_{in}(z) = -C_2 \cdot [1 - z^{-1}] \cdot V_{out}(z)$$
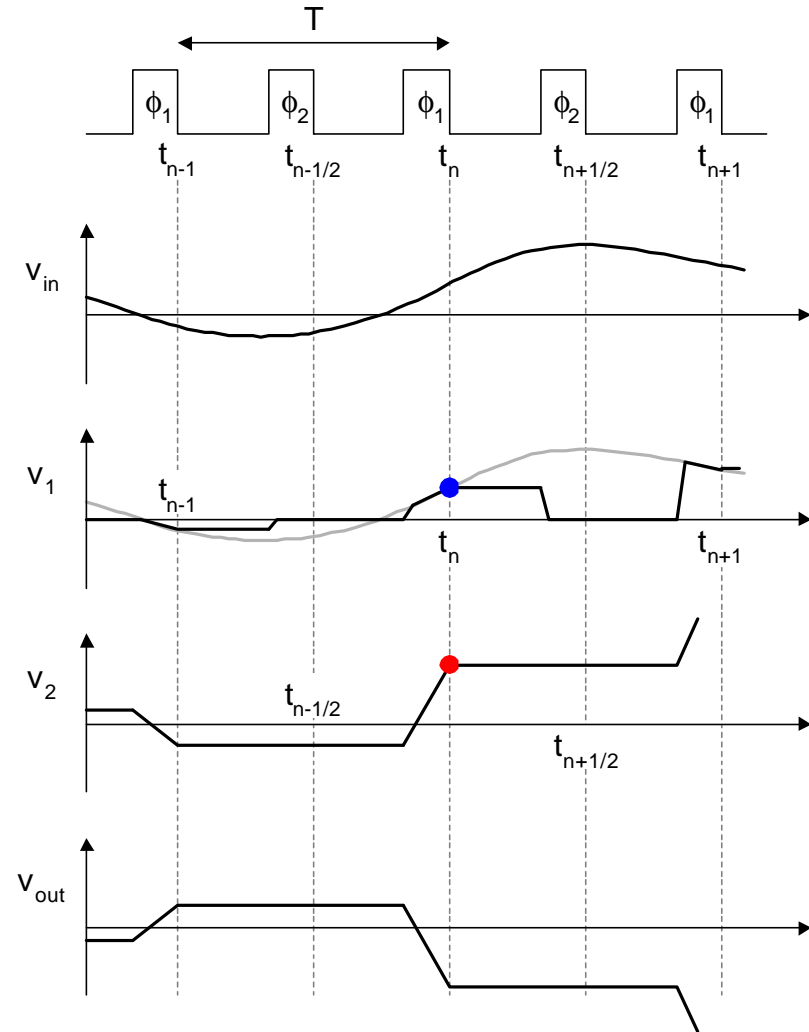
$$\therefore H(z) \equiv \frac{V_{out}(z)}{V_{in}(z)} = -\frac{C_1}{C_2} \cdot \frac{1}{1 - z^{-1}}$$



Frequency Response of SCI

- Transfer Function

$$H(e^{j\Omega T}) \equiv H(z)|_{z=e^{j\Omega T}} = -\frac{C_1}{C_2} \cdot \frac{1}{e^{j\Omega T} - 1}$$

- Condition : **WT << 1**

$$H(e^{j\Omega T}) \cong -\frac{C_1}{C_2} \cdot \frac{1}{\left(1 + j\Omega T - \frac{1}{2}(\Omega T)^2 - \dots\right) - 1} \cong -\frac{C_1}{C_2} \cdot \frac{1}{j\Omega T}$$

- Continuous-Time Integrator


$$H(j\Omega) \equiv H(s)|_{s=j\Omega} = -\frac{1}{R_1 C_2} \cdot \frac{1}{j\Omega}$$

C₁/C₂ & T accurate

- For Same Frequency Response

$$C_1 = \frac{T}{R_1}$$


Parasitic Capacitance Problem

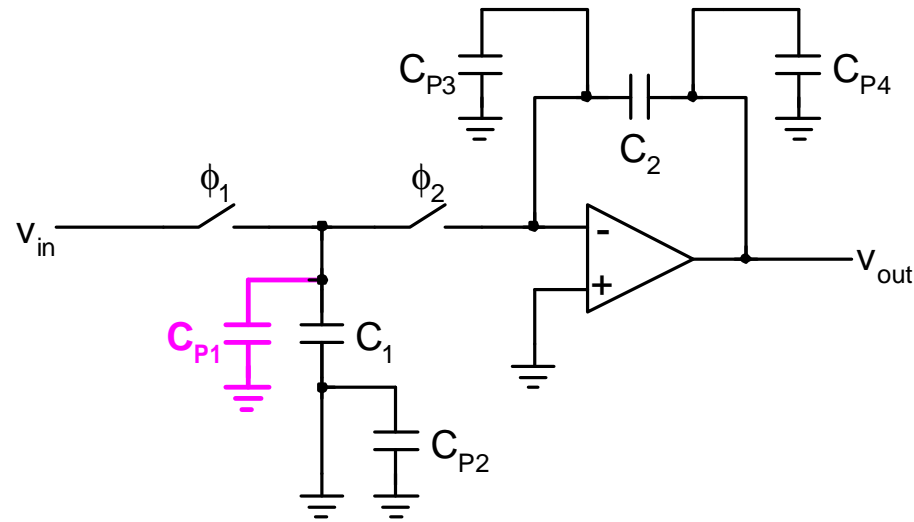

$$\checkmark C_{P1} \rightarrow H(z) = -\frac{C_1 + \mathbf{C_{P1}}}{C_2} \cdot \frac{z^{-1}}{1 - z^{-1}}$$

- ✓ C_{P2} : Connected to GND
- ✓ C_{P3} : Connected to Virtual GND
- ✓ C_{P4} : Connected to Output of an Amplifier

Parasitic-Insensitive SC Integrators

 


$$H(z) \equiv \frac{V_{out}(z)}{V_{in}(z)} = + \frac{C_1}{C_2} \cdot \frac{z^{-1}}{1 - z^{-1}}$$

$$H(z) \equiv \frac{V_{out}(z)}{V_{in}(z)} = - \frac{C_1}{C_2} \cdot \frac{1}{1 - z^{-1}}$$

All Parasitic Capacitors Connected to

- GND / Virtual GND
- Voltage Source / Output of Amplifier

Signal Flow Graph Establishment

 

- Switched- C_1 Branch \rightarrow Input : $V_{in}(z)$, Output : $DQ(z)$

$$\Delta q(n) = q(n) - q(n-1) = C_1 \cdot [0 - v_{in}(n)]$$

$$\Delta Q(z) = -C_1 \cdot z^{-1} \cdot V_{in}(z)$$


- Op Amp w/ Feedback $C_2 \rightarrow$ Input : $DQ(z)$, Output : $V_{out}(z)$,

$$v_{out}(n) - v_{out}(n-1) = -\Delta q(n)/C_2$$

$$V_{out}(z) = -\frac{1}{C_2 \cdot (1 - z^{-1})} \cdot \Delta Q(z)$$




Signal Flow Graph for SC Integrators

 


$$V_{\text{out}}(z) = -\frac{C_1}{C_F} \cdot V_1(z) + \frac{C_2}{C_F} \cdot \frac{z^{-1}}{1 - z^{-1}} \cdot V_2(z) - \frac{C_3}{C_F} \cdot \frac{1}{1 - z^{-1}} \cdot V_3(z)$$

1st-Order SC Filter


- Active RC Version

 

- SC Version

 

- Signal Flow Graph

 


$$H(z) \equiv \frac{V_{out}(z)}{V_{in}(z)} = - \frac{\frac{C_1 + C_2}{C_F} - \frac{C_1}{C_F} z^{-1}}{1 + \frac{C_3}{C_F} z^{-1}}$$




High-Order Filter Implementation

- Cascade of Biquad Blocks

 

$$H(z) = \prod_{i=1}^{N/2} H_i(z) = \prod_{i=1}^{N/2} \frac{b_2 z^2 + b_1 z + b_0}{a_2 z^2 + a_1 z + a_0}$$

- RLC Prototype

 


$$I_2(s) = \frac{1}{sL_2} \cdot [V_1(s) - V_2(s)]$$

$$I_2(z) = I_2(s) \Big|_{s=\frac{2z-1}{Tz+1}}$$


Low-Q SC Biquad

- Active RC Version

 


$$H(s) \equiv \frac{V_{out}(s)}{V_{in}(s)} = - \frac{h_2 s^2 + h_1 s + h_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

- SC Version

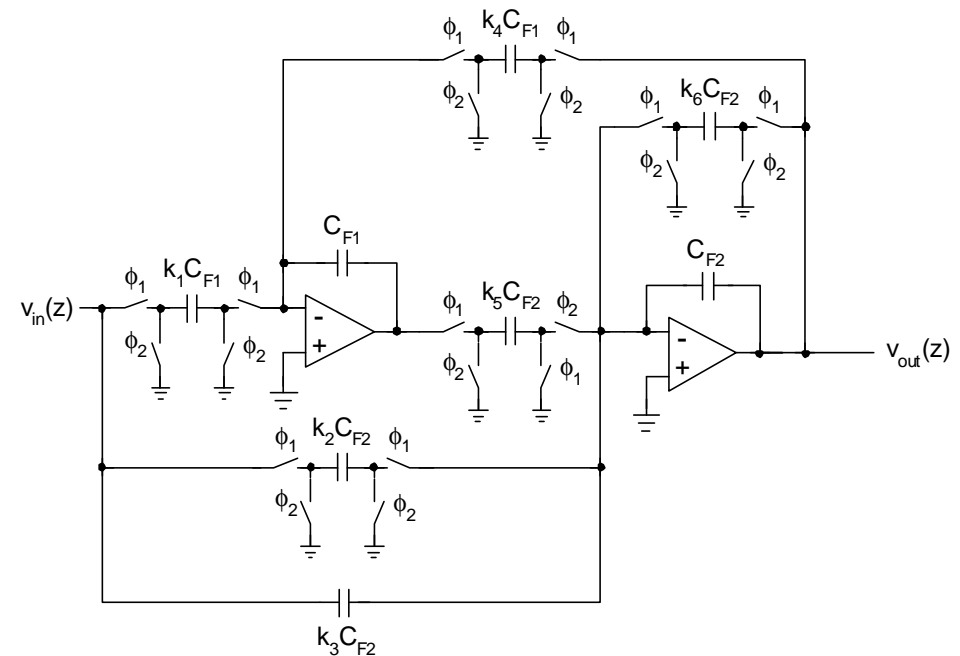

Low-Q SC Biquad (cont' d)

• Signal Flow Graph

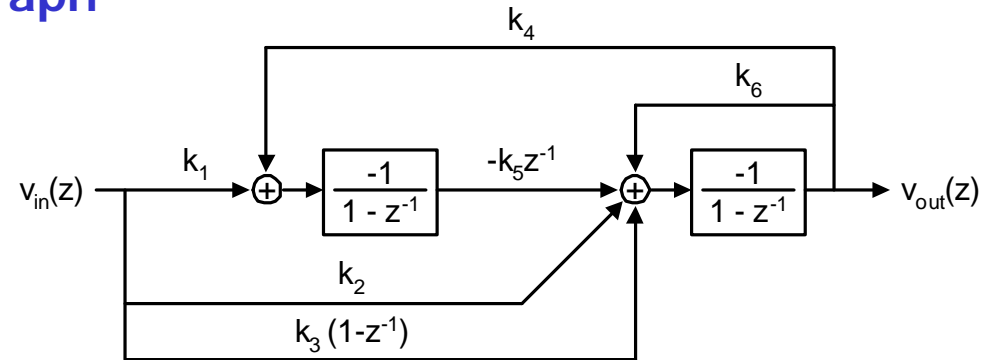

• Transfer Function

$$H(z) \equiv \frac{V_{\text{out}}(z)}{V_{\text{in}}(z)} = -\frac{(k_2 + k_3)z^2 + (k_1 k_5 - k_2 - 2k_3)z + k_3}{(1 + k_6)z^2 + (k_4 k_5 - k_6 - 2)z + 1} = -\frac{a_2 z^2 + a_1 z + a_0}{b_2 z^2 + b_1 z + 1}$$

$$k_3 = a_0$$

$$k_2 = a_2 - a_0$$


$$k_1 k_5 = a_0 + a_1 + a_2$$

$$k_6 = b_2 - 1$$

$$k_4 k_5 = 1 + b_1 + b_2$$


High-Q SC Biquad

- Active RC Version

 


$$H(s) \equiv \frac{V_{out}(s)}{V_{in}(s)} = -\frac{h_2 s^2 + h_1 s + h_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

- SC Version

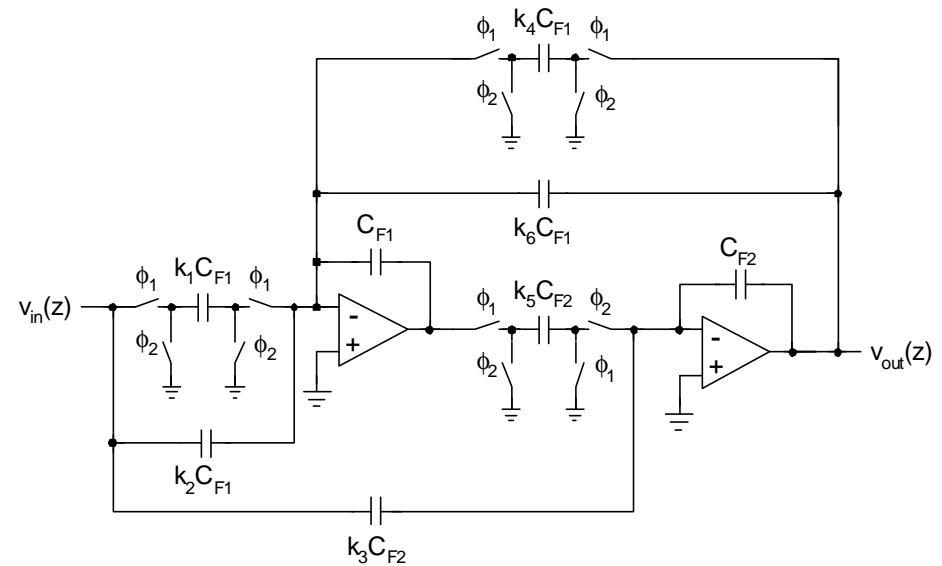

High-Q SC Biquad (cont' d)

● Signal Flow Graph

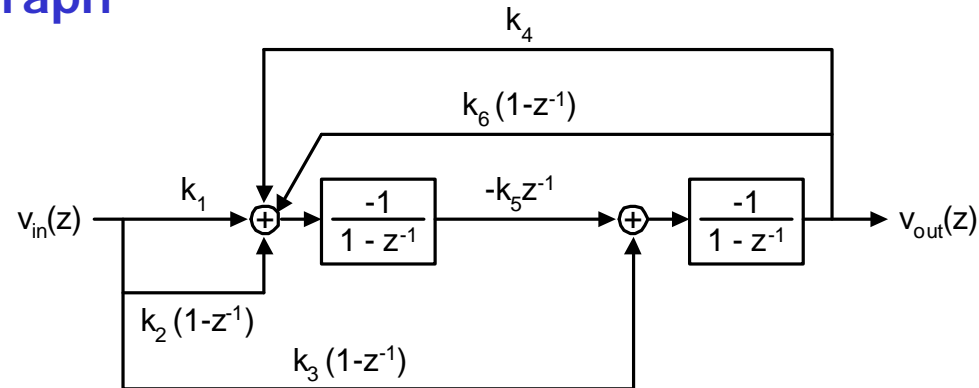

● Transfer Function

$$H(z) \equiv \frac{V_{\text{out}}(z)}{V_{\text{in}}(z)} = -\frac{k_3 z^2 + (k_1 k_5 + k_2 k_5 - 2k_3)z + (k_3 - k_2 k_5)}{z^2 + (k_4 k_5 + k_5 k_6 - 2)z + (1 - k_5 k_6)} = -\frac{a_2 z^2 + a_1 z + a_0}{z^2 + b_1 z + b_0}$$

$$k_3 = a_2$$

$$k_2 k_5 = a_2 - a_0$$


$$k_1 k_5 = a_0 + a_1 + a_2$$

$$k_5 k_6 = 1 - b_0$$

$$k_4 k_5 = 1 + b_1 + b_0$$

SC Ladder Filter

- RLC Prototype

 


$$-V_1 = -\frac{1}{sC_1} \cdot \left[\frac{V_{in} + (-V_1)}{R_s} + (-I_2) \right]$$

$$-I_2 = -\frac{1}{sL_2} \cdot (V_1 - V_3)$$


$$V_3 = -\frac{1}{sC_3} \cdot \left[(-I_2) + \frac{V_3}{R_L} \right]$$

- CT Block Diagram

 

SC Ladder Filter (cont' d)

- Active RC Implementation

 



$$C_S \rightarrow T/R_S$$

$$C_L \rightarrow T/R_L$$


$$C \rightarrow T/1$$

- SC Implementation

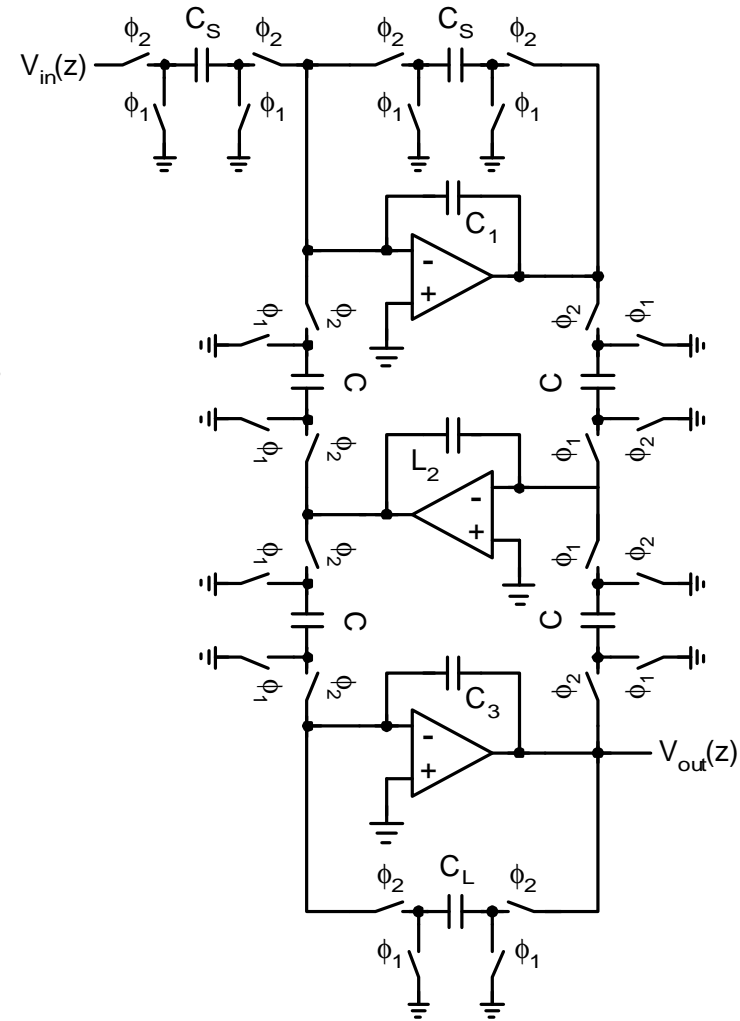

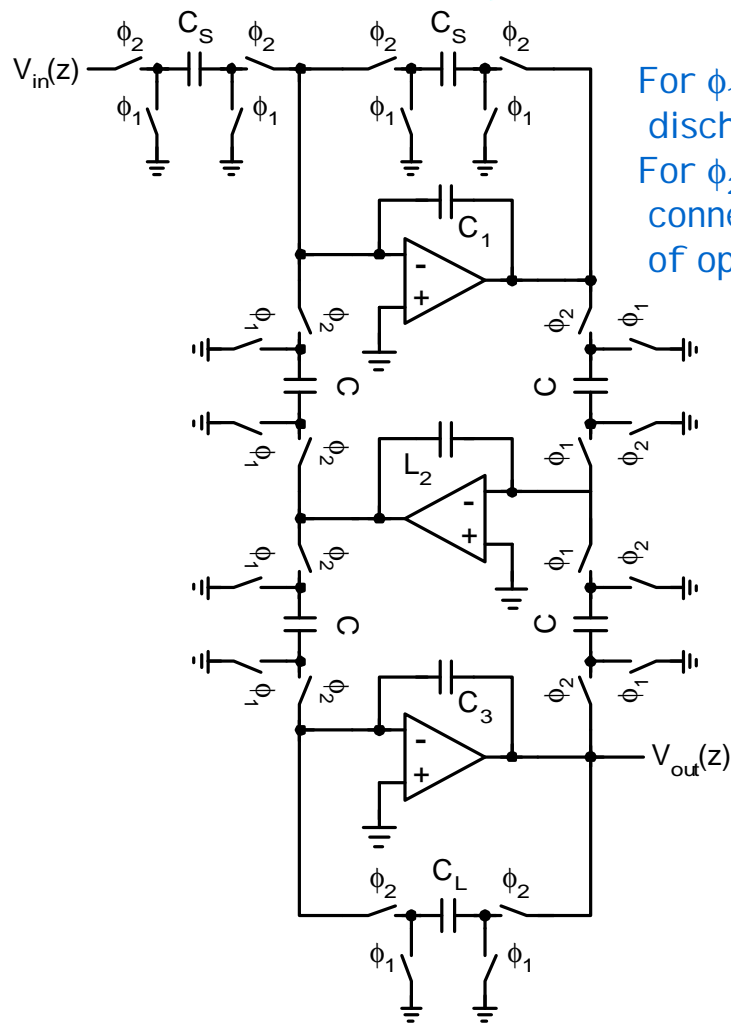

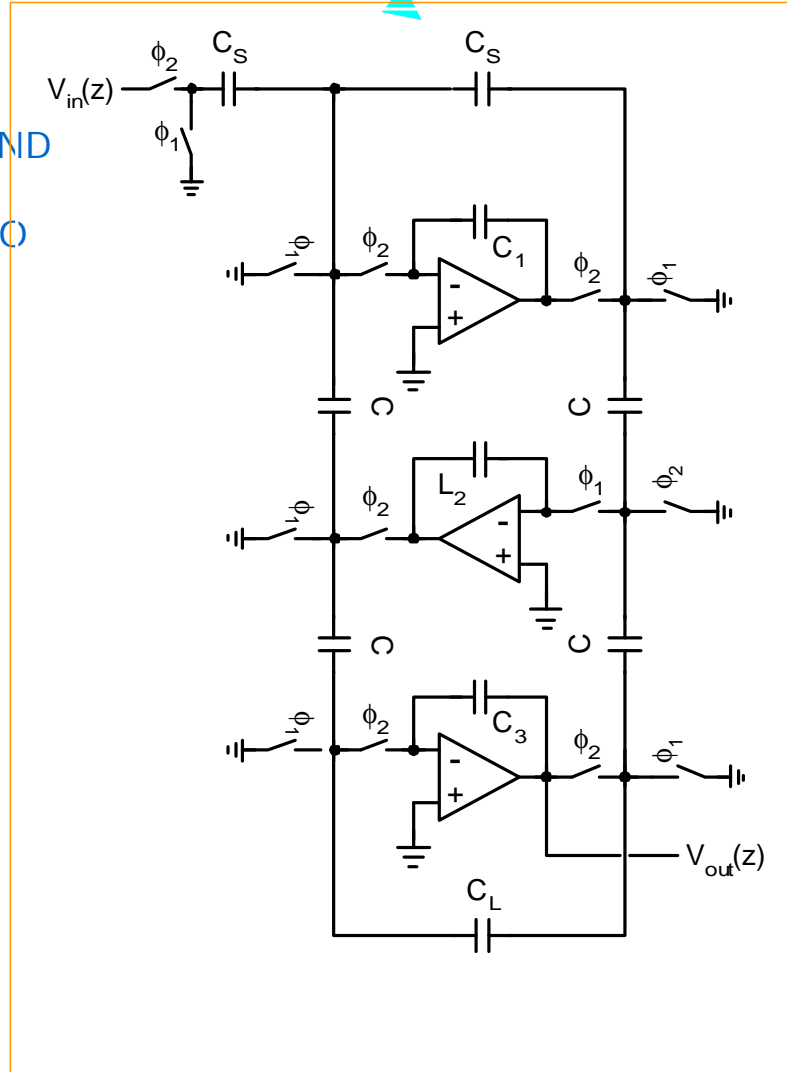For ϕ_1
 discharged to GND
 For ϕ_2
 connected to I/O
 of op amp.




Scaling for Maximum Dynamic Range

- Capacitors Connected to Output of Op Amp k , $C_{m,k}$

$$C_{m,k} \cdot \alpha_k \rightarrow V_{out,k} / \alpha_k$$

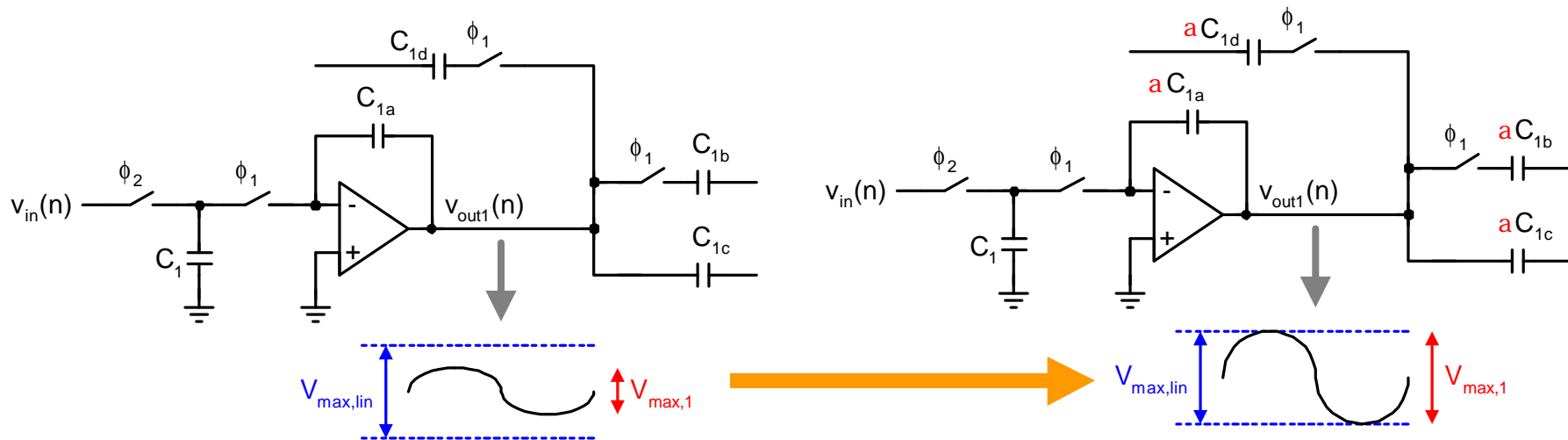- For Maximum Output of Op Amp k , $V_{max,k}$ $a_k = V_{max,k} / V_{max,lin}$



- Noise Increase by Much Less than $O(a_k)$

Scaling for Minimum Capacitance

- Capacitors Connected to Input of Op Amp k , $C_{n,k}$

$$C_{n,k} \cdot \beta_k \rightarrow V_{in,k}$$

- For Minimum Capacitance of Op Amp k , $C_{min,k}$

$$\beta_k = C_{min} / C_{min,k}$$

where C_{min} is the min. capacitance value set by technology.

- Smallest Capacitor Connected to Input of Op Amp $k \sim C_{min}$
- Total Capacitance Minimized



Non-ideal Problems in SC Filters

- **Switch Nonidealities**

- ✓ Non-Zero On-Resistance
- ✓ Charge Injection
- ✓ Junction Leakage Current

- **Capacitance Nonidealities**


- ✓ Mismatch Problem

- **Op Amp Nonidealities**

- ✓ Offset Voltage
- ✓ Finite DC Gain & Bandwidth
- ✓ Limited Slew Rate
- ✓ Non-Zero Output Impedance
- ✓ Noise



Charge Injection

 

- Due to Overlap Capacitance C_{OV} → Signal Independent


$$\Delta V_{OV} = -\frac{C_{OV}}{C_1 + C_{OV}} \cdot (V_{DD} - V_{SS})$$

- Due to Channel Charge DQ_{CH} → Signal Dependent

$$\Delta V_{CH} = \frac{\Delta Q_{CH}/2}{C_1} = -\frac{C_{ox} WL (V_{GS} - V_{TH})}{2C_1} = -\frac{C_{ox} WL (V_{DD} - V_S - V_{TH})}{2C_1}$$

Solution - ΔV_{OV}

 
- Half-Size Dummy Switch Driven By Complement Clocks
- Transmission Gate
- Fully Differential Approach



→ $\Delta V_{OV}^{(+)}$ & $\Delta V_{OV}^{(-)}$ Cancelled Each Other

Solution - DV_{CH}

• Delayed Clocking Scheme

 


- ✓ Due to S_1 : Channel Charge Dependent on V_{in}
- ✓ Due to S_3 & S_4 : Channel Charge Dependent on GND
 - ➔ Can be Removed
- ✓ Turning Off S_3 & S_4 Earlier ➔ Channel Charge of S_1 Isolated from C_2

• Using Compensation Capacitor

- ➔ Insert $(-)\Delta Q_{CH}$ Stored on Compensation Capacitor



Capacitance Mismatch

 - Area Inaccuracy & Oxide Thickness Variation
- Keep Capacitance Ratio Constant



$$\frac{C_2}{C_1} = \frac{(40 - 0.5) \cdot (40 - 0.5)}{(20 - 0.5) \cdot (20 - 0.5)} = 4.103$$


← 2.6% error

  


$$\frac{C_2}{C_1} = \frac{4(20 - 0.5) \cdot (20 - 0.5)}{(20 - 0.5) \cdot (20 - 0.5)} = 4$$

Capacitance Layout

- Commom-Centroid Approach

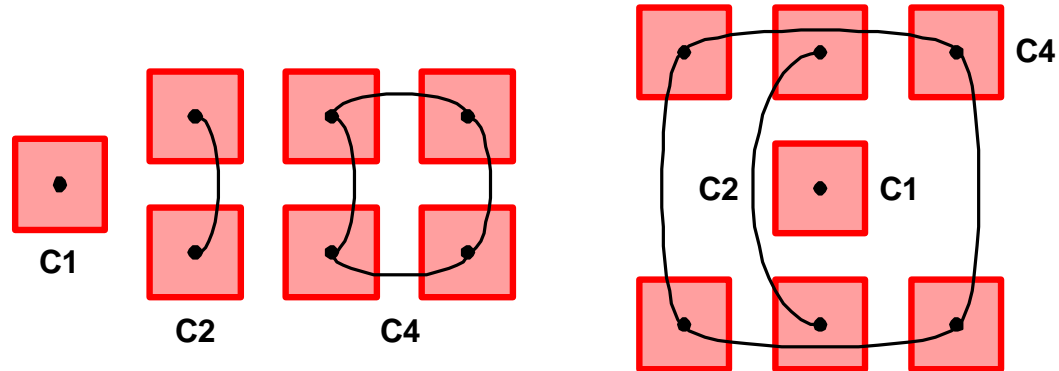

- Ground Shielding

 


CDS Technique


- Correlated Double Sampling

- Can Remove

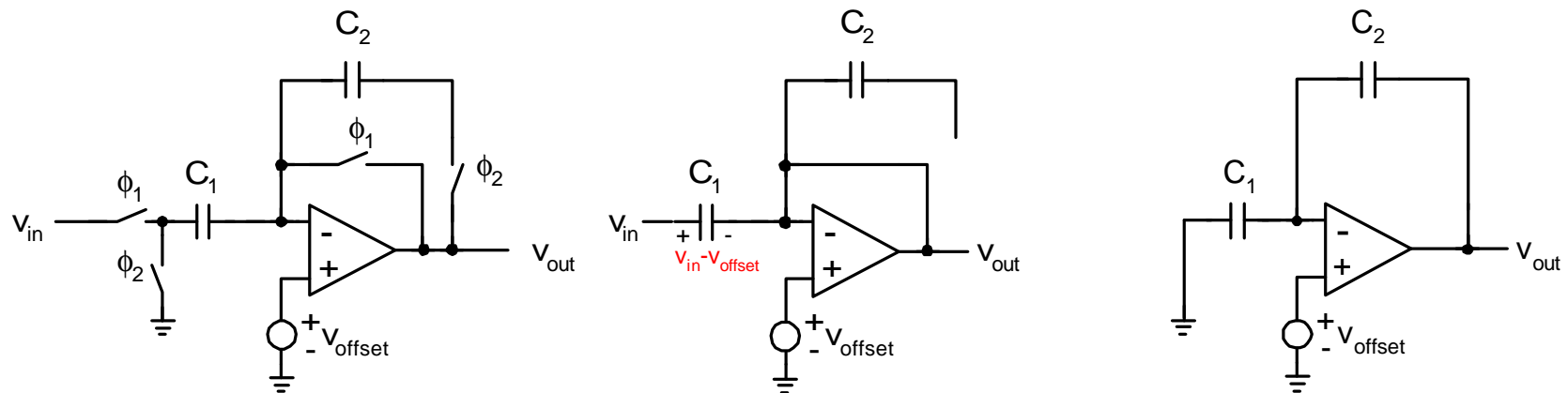Offset Voltage, 1/f-Noise, Power Supply Noise, Finite DC Gain Error



Finite DC Gain of Op Amp

 

- Transfer Function

$$H(z) = -\frac{C_1/C_2}{\left(1 + \frac{1 + C_1/C_2}{A_0}\right) - \left(1 + \frac{1}{A_0}\right)z^{-1}}$$

- Frequency Response

$$H(e^{j\omega T}) = \frac{H_{\text{ideal}}(e^{j\omega T})}{1 - m(\omega) - j\theta(\omega)} = -\frac{C_1}{C_2} \cdot \frac{e^{j\omega T/2}}{j\sin(\omega T/2)} \cdot \frac{1}{1 - m(\omega) - j\theta(\omega)}$$

- Magnitude Error

$$m(\omega) = -\frac{1 + C_1/2C_2}{A_0}$$


- Phase Error

$$\theta(\omega) = \frac{C_1/C_2}{2A_0 \sin(\omega T/2)}$$

Finite Bandwidth of Op Amp

- Op Amp : One-Pole System w/ Unity Gain Freq. of ω_0
 
$$A_V(s) = \frac{A_0}{1+s/p_1} = \frac{A_0 \cdot p_1}{s+p_1} = \frac{\omega_0}{s+p_1}$$



- Frequency Response

$$H(e^{j\omega T}) = F(\omega) \cdot H_{\text{ideal}}(e^{j\omega T}) = -\frac{C_1}{C_2} \cdot \frac{e^{j\omega T/2}}{j \sin(\omega T/2)} \cdot F(\omega)$$


- Magnitude Error

$$|F(\omega)| = 1 + m(\omega) = 1 - e^{-\frac{C_2}{C_1+C_2} \frac{\omega_0 T}{2}} \left(1 - \frac{C_2}{C_1 + C_2} \cos(\omega_0 T) \right)$$

- Phase Error

$$\angle F(\omega) = \theta(\omega) = -e^{-\frac{C_2}{C_1+C_2} \omega_0 T/2} \cdot \frac{C_1}{C_1 + C_2} \sin(\omega_0 T)$$

Layout Example

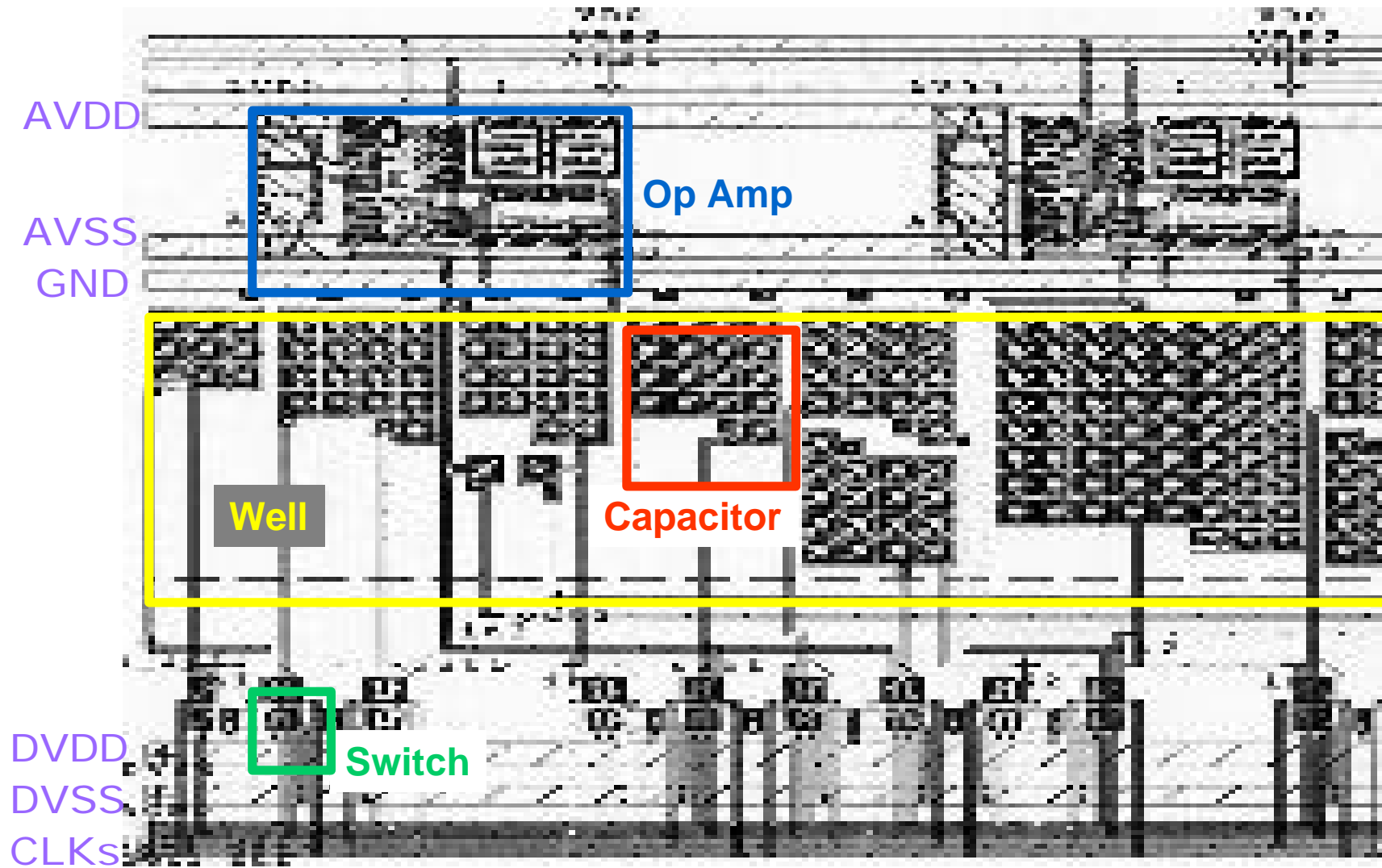


SC Filter Simulation Example

■ Low-Q SC Lowpass Biquad Filter


FFT Analysis for Each Frequency of Interest

```
.fft v(node) np = 2048 format = unorm
```

● Circuit Schematic

 


● Simulation Results

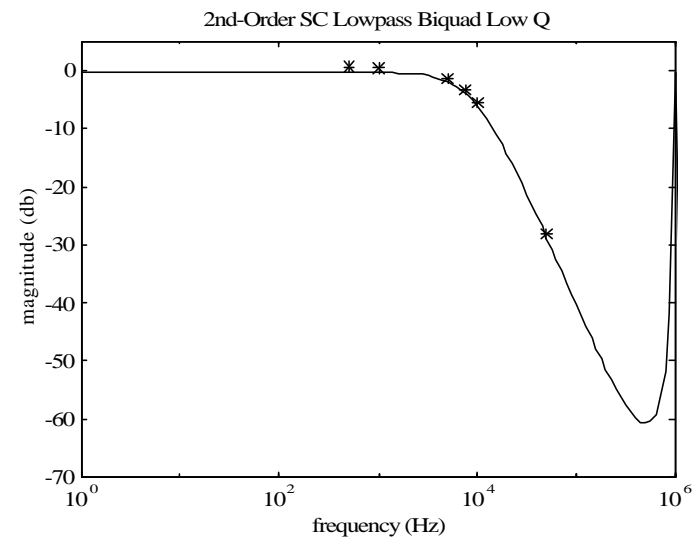



Implementation Example

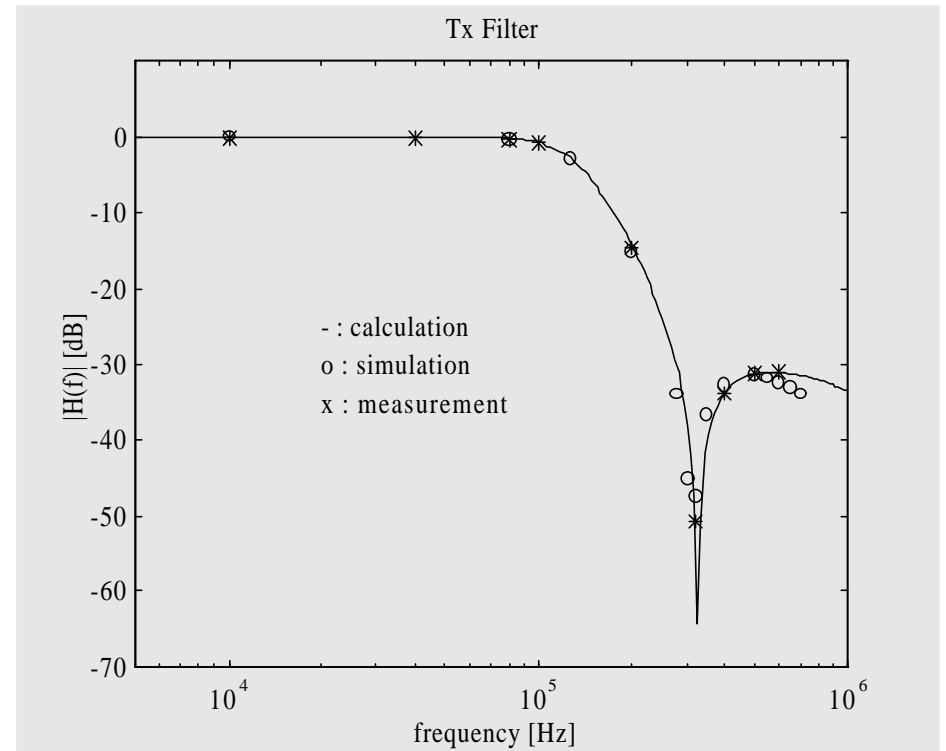5th-Order Lowpass Filter for ISDN U-I/F AFE




Recent Advance Example 1

6th-Order Channel Select Lowpass Filter

  


2.1 mm

 

 *IEEE VLSI Symposium 1996.*

Recent Advance Example 2

 Bandpass Biquad w/ Gain-Enhancement Replica Op Amp



$$A=C=1 \quad B=D=1.613 \quad G=E=0.1613 \text{ (T-network)}$$



$$f_{\text{center}} = 10\text{MHz} \quad (Q=10)$$

$$f_{\text{sample}} = 100\text{MHz}$$

 IEEE ISSCC 1997.

Recent Advance Example 3

Bandpass Biquad w/ Switched Op Amp

 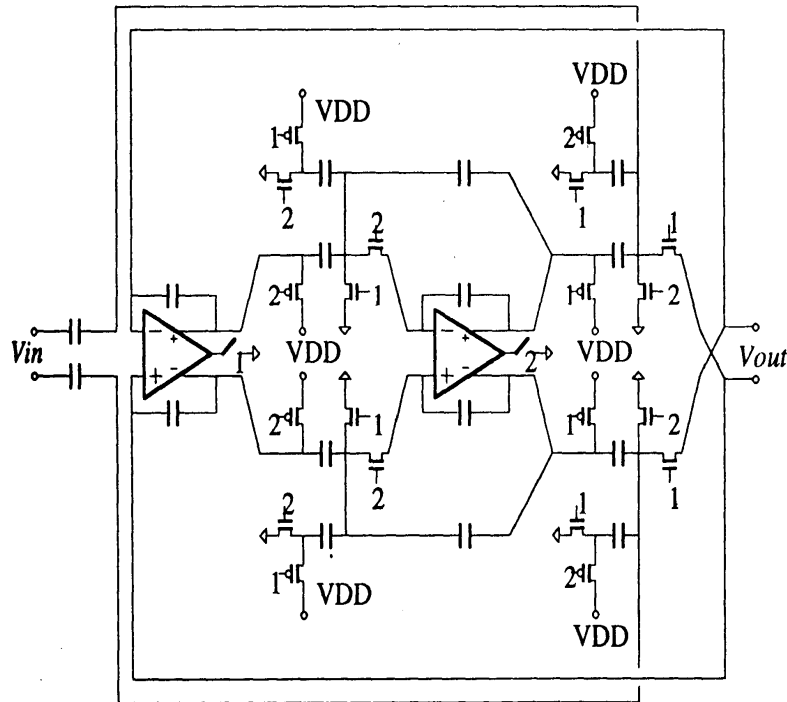

$$f_{center} = 440\text{kHz} (Q=6.7) \text{ w/ } f_s = 1.8\text{MHz}$$


$$\text{Power} = 160\mu\text{W} @ V_{DD}=1\text{V}$$

 IEEE ISSCC 1997.



Recent Advance Example 4

200MSampes/s SC-LPF

 


0.5- μm CMOS Technology

Power = 10mW @ $V_{DD}=3\text{V}$

 IEEE ISSCC 1999.

Recent Advance Example 5

1V SC-BPF w/ Switched Op Amp

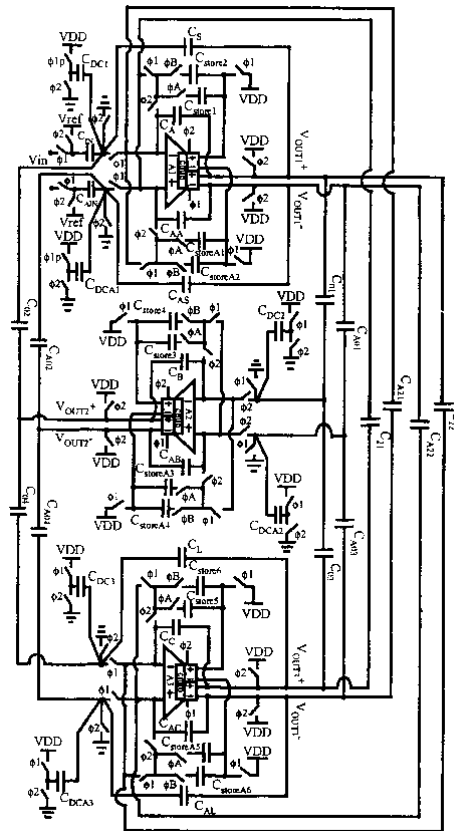

0.5- μm CMOS Technology

$f_o = 75\text{kHz}$ w/ $Q = 45$

Power = $310\mu\text{W}$ @ $V_{DD}=1\text{V}$

 IEEE ISSCC 2000.